



# Diodes properties and characteristics

Science That benefits

01  
تذكير

02  
شرح منحني  
مميزة الدايود

03

04


الدايود المثالي  
و الدايود الحقيقي

سلوك الدايود  
في دائرة التيار  
المستمر



# خواص الدايود : Diode


الصمام المثالي: IDEAL DIODE

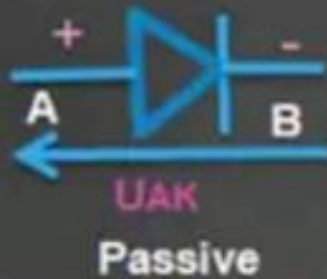

If  $V_A$  anode potential and  $V_B$  cathode potential

The diode is forward biased

The diode is Reverse biased

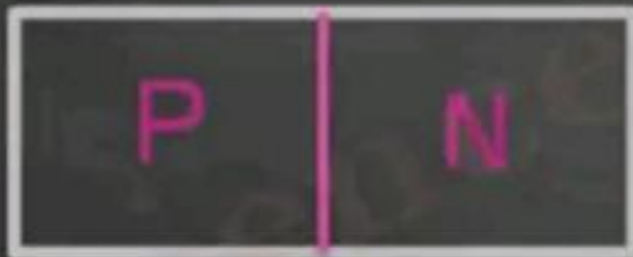


PN - junction



Active

# Characteristics voltage- current

شرح منحنى ميزة الدايود:

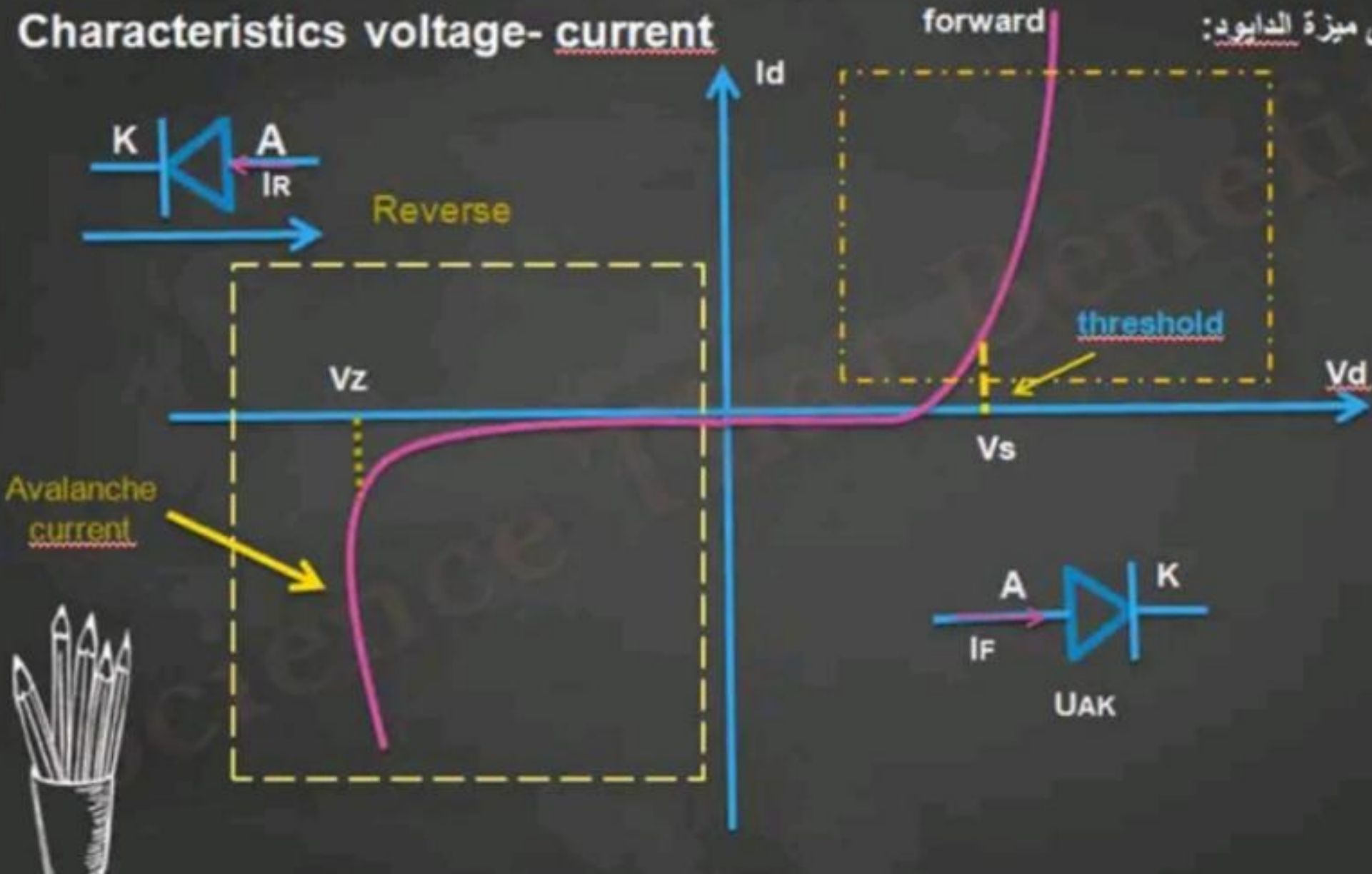

## Ideal Diode behavior modelling



في حالة الدايود مثالي :

$$V_S = 0$$

$R_S$  مقاومة الدايود معدومة ، يعتبر كقاطع مغلقة  
 $R_S$  مقاومة الدايود كبيرة جدا ، يعتبر كقاطع مفتوحة

## real Diode behavior modelling :

The dynamic resistor assumed to be constant  $r_d$


Ideal Diode :  $r_d = 0$  ;  $V_S = 0$  short circuit (first approximation ).

Real Diode :

$r_d = 0$  ;  $V_S \neq 0$  ;  $V_S$  voltage generator ( second approximation ) .


$R_d \neq 0$  ;  $V_S \neq 0$  ; voltage generator  $V_S$  and  $r_d$  dynamic resistor ( third approximation ) .

$$V_D = V_S + r_d \cdot I$$

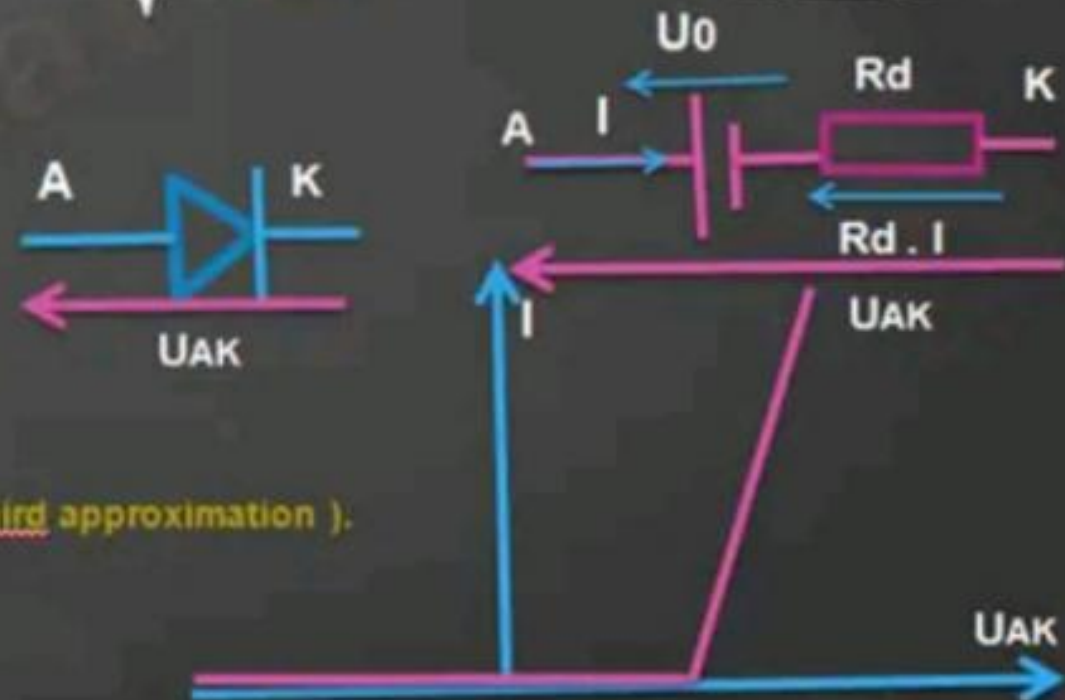





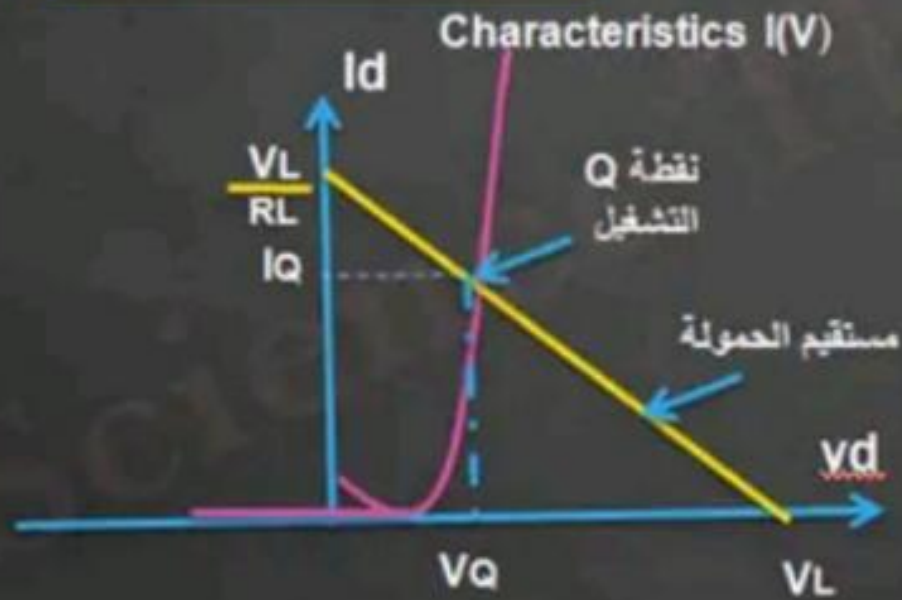سلوك الصمام الثنائي في دوائر التيار المستمر:



$$\begin{aligned} V_{Th} &= V_S \\ R_{Th} &= R_S + R_L \\ r_s &= \frac{V_D}{I_D} \end{aligned}$$

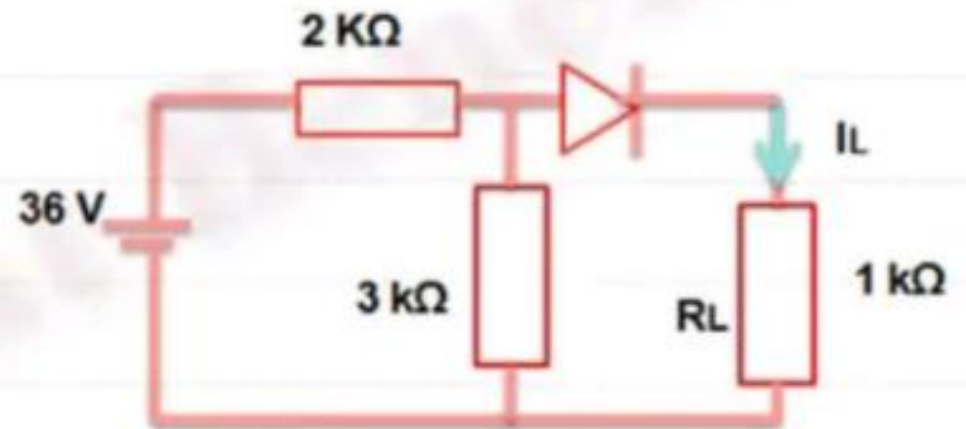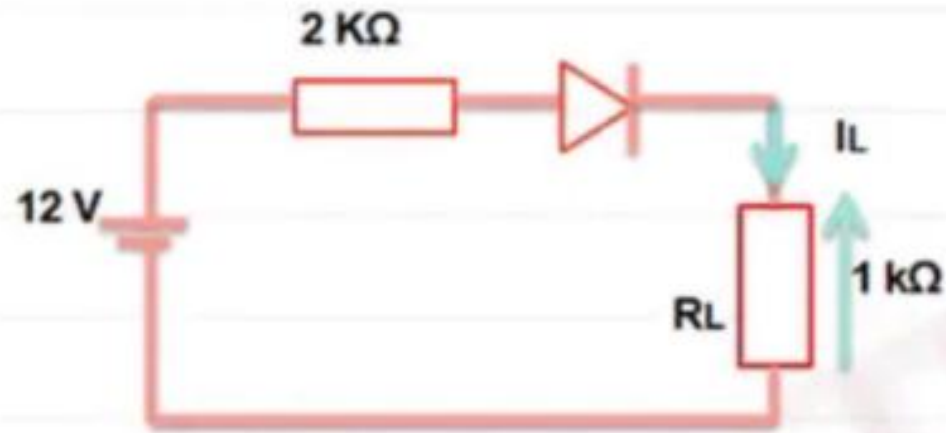**EXAMPL :** Determine the current and the voltage in the Load  $R_L$ , in the following circuits.  
 $V_s = 0.7 \text{ V}$ ,  $r_d = 0.23 \Omega$




**Solution**

1 in the first circuit:

$V_D > 0.7 \text{ V}$  the threshold voltage, the diode is ON (short circuit)

USING the first approximation  $\Leftrightarrow$

Replace the Diode (short circuit)

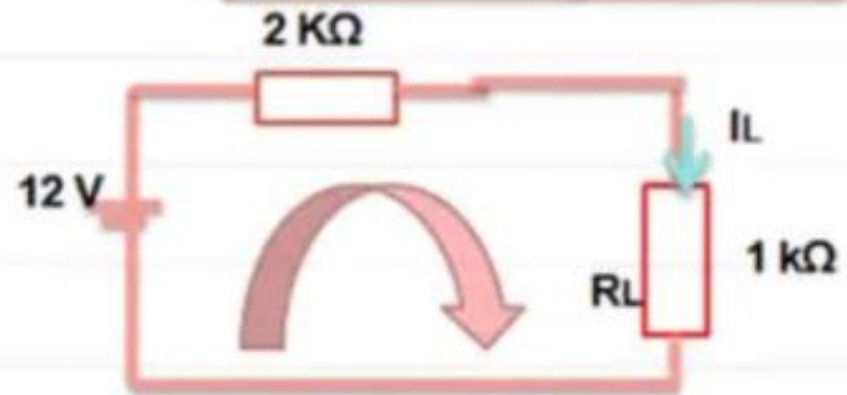

### 1. THE current ACROSS RL

$$V_{CC} - 2 \text{ k}\Omega \times I_L - V_D - R_L \cdot I_L = 0$$

$$12\text{V} - 2 \text{ k}\Omega \times I_L - R_L \cdot I_L = 0$$

$$12 = I_L \cdot (2000 + 1000) \Rightarrow I_L = 12 / 3000 = 4 \text{ mA}$$


### 2. the voltage Between RL:

$$V_L = R_L \cdot I_L$$

$$V_L = 1 \text{ k}\Omega \times 0.004 = 4 \text{ V}$$



$V_D ?$

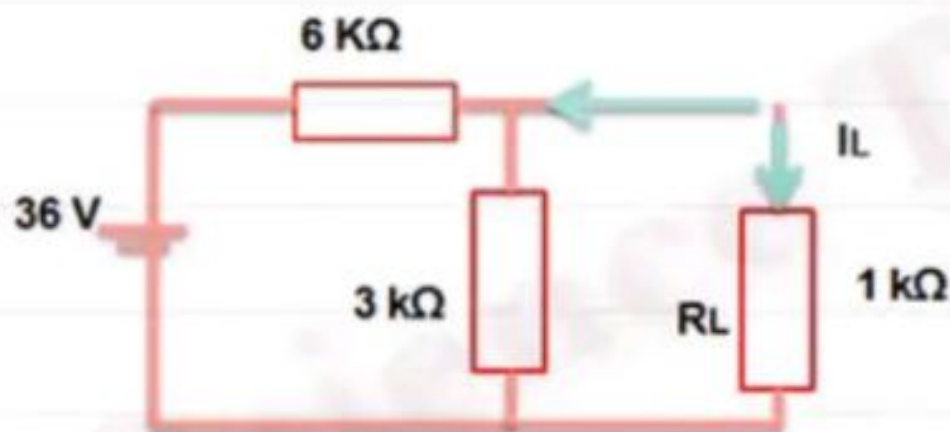

### 1. Using voltage divider :

$$V_D = \frac{3}{3 + 6} \times 36 = 12 \text{ V}$$

$V_D > V_S \Rightarrow$  Diode is forward Bias (passante)

### 2. Using thevenin's theorem :


$$V_{th} = \frac{3}{3 + 6} \times 36 = 12 \text{ V}$$

$$R_{th} = \frac{6 \cdot 3}{6 + 3} = 2 \text{ k}\Omega$$





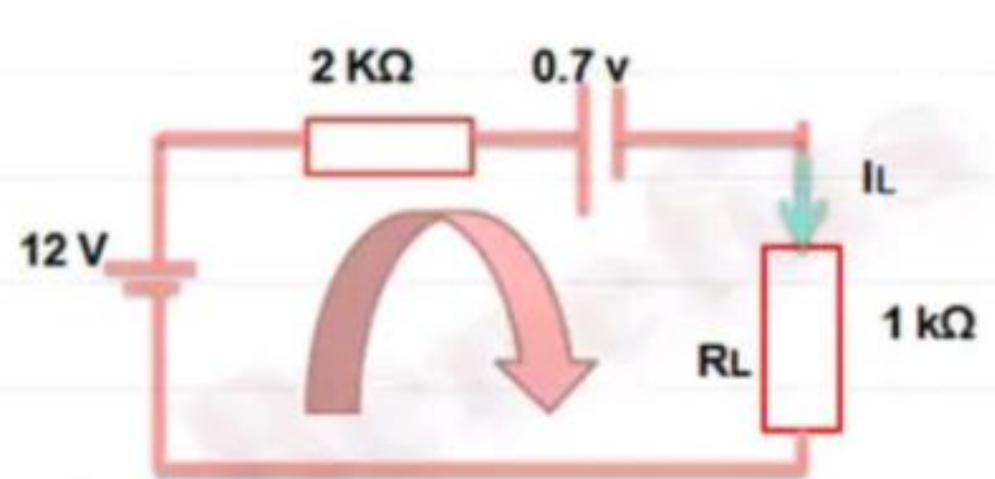The Diode is replaced by a voltage generator



Using KVL :

$$V_{th} - R_{th} \cdot I_L - V_d - R_L \cdot I_L = 0$$


$$12 - 2 \times I_L - 0.7 - 1000 \cdot I_L = 0$$

$$11.3 = I_L (2000 + 1000) \Rightarrow I_L = \frac{11.3}{3000} = 3.7 \text{ mA}$$

$$V_L = I_L \cdot R_L = 3.7 \cdot 1000 \cdot 1 = 3.7 \text{ V}$$



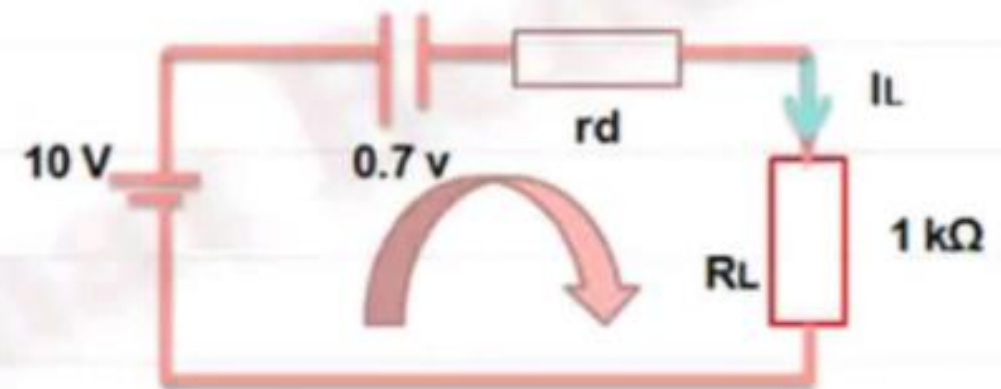$V_D = 10\text{ V} \Rightarrow$  the diode is forward biased  
 Using the third approximation ( diode replaced by  
 voltage generator  $0.7\text{ v}$  and dynamic resistor  $r_d = 0.23\ \Omega$



Using KVL:

$$10 - 0.7\text{ V} - r_d \cdot I_L - R_L \cdot I_L = 0$$

$$9.3 = I_L \cdot (r_d + R_L)$$

$$I_L = \frac{9.3}{0.23 + 1000} = 9.29\text{ mA}$$

$$V_L = \frac{9.29 \times 1000}{1000} = 9.29\text{ V}$$